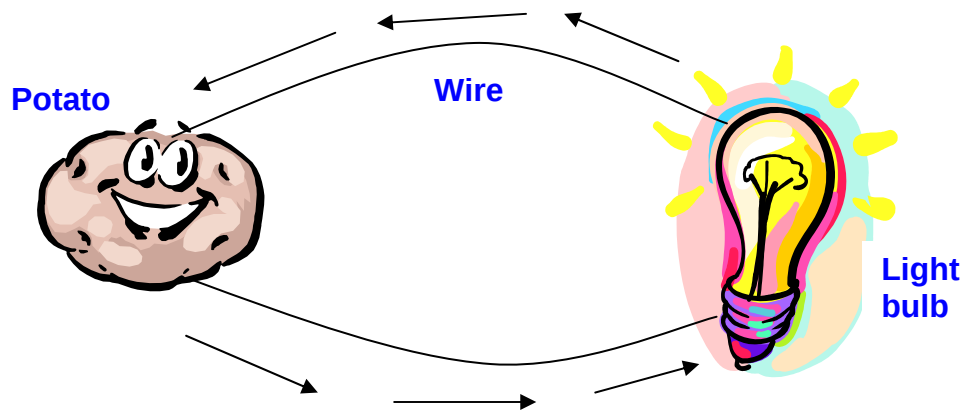


Make a Battery Worksheet



Answers

1. Draw a picture of the potato battery setup in the space below. Label the **potato**, **wire**, and **light bulb** parts. Draw **arrows** to show the direction of the current.



2. How does the potato help the circuit to work?

Potatoes give the electrons a solution to help them
move to the copper to the zinc, and complete the
circuit.

3. Why must engineers understand circuits when making electrical appliances?

Engineers need to understand circuits in order to
force electrical energy flow through the right
resistors in technologies that run off electricity.